

Mysteries of Wang Magnetic Memory


Douglas Miller <durgadas311@gmail.com>

April 11, 2024

This journey began when I noticed something odd about the timing of signals used to access the Wang 500/600 microcode ROM. The signal timing did not match my understanding of how the ROM worked.


As background, the basic “wire-weave” ROM technology is as follows. Each word of microcode is represented by a single wire that is woven through transformers (one for each bit) such that a “1” is represented by the wiring passing inside the given transformer. When a wire is activated (energized), it produces a pulse in the transformer, using the basic principals of electro-magnetism ([Faraday’s Law of Induction](#)). When the wire is first energized, it produces a negative pulse, and when the wire is de-energized it produces a positive pulse. The negative pulse is destructive to the digital circuitry and so must be shunted through a diode to protect that.

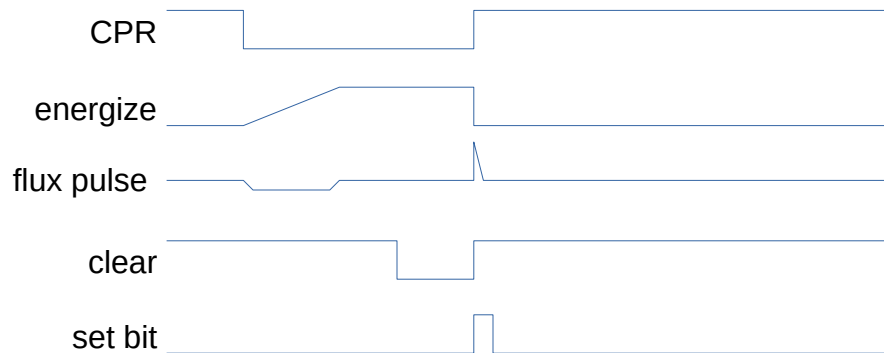The Wang 700 ROM signals match my expectations. The leading edge of the energizing signal is “softened” by slowing the rise time, such that a minimal negative pulse is generated through the shunt diode. The falling edge of the signal produces the positive pulse used to set a “1” in the respective bit positions. The timing of the signals is as follows:




Note how the “clear” signal, which is required to clear the data latches before setting the “1” bits, precedes the end of the CPR (energizing) signal, such that it does not conflict with the pulses that set “1”.

The Wang 500/600 signals are different. The CUP signal, used to energize the wire, and the CL (clear) signals begin at the same time. The transformer outputs (and SET latch inputs) are normally held to ground through a diode by the inactive state of the ST signal, presumably to prevent noise from corrupting the results during the rest of the instruction cycle. But, the ST signal only enables the latches before the end of the energizing signal, and so the positive pulse resulting from the trailing edge of CUP cannot set the latches. Here are the timing signals:

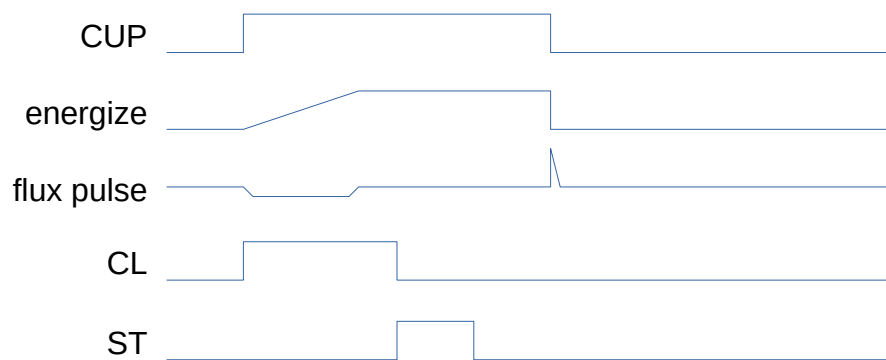

So, the question is how can the “normal” pulse generated at the end of the CUP signal be used to set latches if those are only enabled during the ST signal which precedes that event. I’ve been over the schematics, and even compared them to hand-drawn schematics I made in 1984 (before official schematics were publicly available). Everything suggests that my interpretation of the signals timing and usage is correct.

I am faced with the possibility that Wang was using some property of electro-magnetism that I don’t understand. This led me to take a detour into magnetic core memory, which Wang used on the 700 models. In conventional core memory, the reading of a bit involves setting the bit to “0” and then detecting (sensing) whether the core changed state in order to do that (i.e. $1 \rightarrow 0$ involves a flux change, while $0 \rightarrow 0$ does not). This is done by writing a “0” to the bit “in the normal way” while using the “sense” wire to detect any induced current from a $1 \rightarrow 0$ transition. The timing of a read from Wang 700 core memory is as follows:

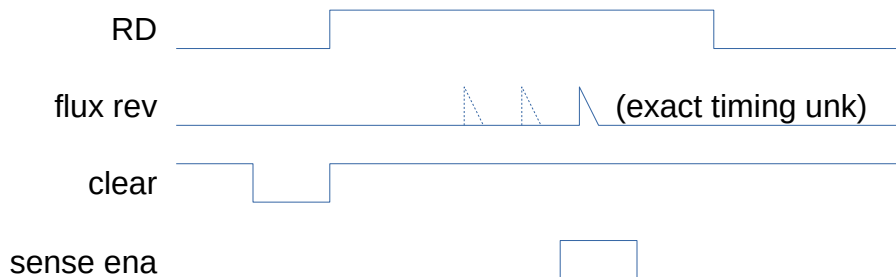

Note how the output latches are cleared early, then the X/Y wires are energized (RD) in order to write a “0”. Notice that the sense amplifier outputs are enabled before the end of energize signals, similar to what is done on the Wang 500/600 ROM. In this case, that is because the core “flips” state some time after the beginning of the energize signal, but is not tied to the end of the energize signal (instead, it is based on the access time of the memory, which depends on design details and materials). It is not clear if the sense enable is precisely timed relative to RD start, or if it only needs to be approximate. It is also not clear to what degree the sense amplifiers might hold a pulse long enough for the sense enable to allow it to pass along to the latches, making the timing less critical. There is no ability to tune or vary the timing of the sense enable signal relative to the RD signal.

One more difference between the wire-weave ROM and magnetic core memory is that the ROM transformers have a true coil as the secondary/sense, which magnifies the effects of the flux changes. Magnetic core memory uses simple sense wires. Also, the cores retain their flux direction after removal of the drive current, so there is no collapsing magnetic field to induce current when the energize signal turns off. The only time the core induces a current is when it changes state (flips direction).

The Wang wire-weave ROMs, supposedly, do not use the same type of materials in the transformer cores as are used for magnetic core memory (so may not have any “memory” side-effect). Although, this is not confirmed. The drive circuitry for the ROM does not use negative current (unlike core memory, which uses +/- current for 0/1), so the transformers (supposedly) could not be detecting a flux-reversal as is done in core memory. However, on the 500/600, the transformer secondary (sense) coils are kept grounded except for during the ST pulse. The magnetic field from the energized wire is present at the time that the coils are ungrounded. So perhaps there is some special effect, such that the existing and steady magnetic field on the energized wire appears to the recently-ungrounded coil as a changing magnetic field, thus inducing a pulse. It is not clear if this has any relationship to “[The Hall Effect](#)”.

Perhaps it will require observing the actual signals on a real Wang 600 to determine what is going on. One difficulty with that is that the impedance of test equipment probes may interfere with operation of the transformer secondaries. It is not known if some special coupling can be used there.

END